
 


Project Milestone 2 Report

Design

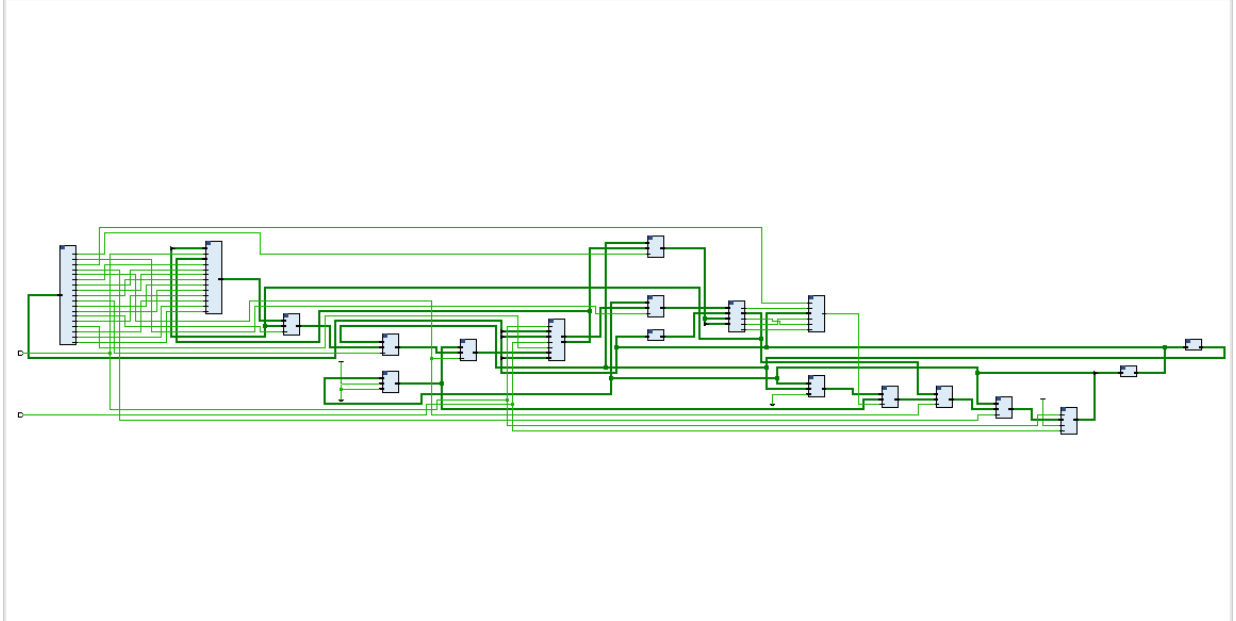

Implementation

We implemented the schematic as the one attached exactly, the only difference was that instead of using a single multiplexor we used three multiplexors to check for the program counter and 4 multiplexors to check the write data that would be written to the register file.

Modules

Instruction_memory: Stores the instruction set for the processor. Given a program counter value, it outputs the corresponding 32-bit instruction.

rv32_ImmGen: Extracts and sign-extends immediate values from the instruction, supporting all RISC-V formats (I, S, B, U, J).

REG_file: Implements the RISC-V register file with 32 general-purpose registers. It allows reading two registers and writing to one per cycle.

Control_unit: Decodes the instruction opcode and function bits to generate control signals for ALU, memory, branching, halting, branching and register file operations

ALU_control: Generates a specific ALU operation code based on the instruction's funct3, funct7, and the general ALUop signal.

prv32_ALU: Performs arithmetic and logical operations like addition, subtraction, AND, OR, shifts, etc. Also sets status flags (zero, carry, sign, overflow).

branchCTRL: Evaluates whether a branch should be taken based on instruction type and ALU flags (zero, sign, carry, overflow).

Data_memory: Implements data RAM for load/store instructions. Supports byte, half-word, and word operations with sign or zero extension.

RCA: A 32-bit Ripple Carry Adder used for address calculations like $PC + 4$ or $PC + \text{immediate}$ for branching and jumping.

Issues Encountered

- Typos in the code caused PC_out to not be updated correctly
 - Typos Fixed.
- ALU_control was outputting wrong ALU selects which caused sub operations to add
 - Fixed ALU select output from the ALU_control to match that in the ALU.
- Instruction memory encoding of test cases contained errors.
 - Added underscored to separate part of the instructions to prevent errors.
- Shifting instructions in r type were incorrect because the input Shift to the LAU was incorrect.
 - Changed it to the output of the multiplexor between the rs2 and the immediate.

Screenshots of test cases attached in the submission github repository

We used multiple programs to test different instructions and we separated these programs in the github repository, we checked that each instruction outputted the correct values whether it was a register value or a value in the memory or a jump and a branch. We concluded that all the results are correct and the screenshots are attached.